

# Traffic Light System

---

Chris Sutton – 6214363



Martin Siddons - 100225776

---

# Traffic Light Controller State Diagram
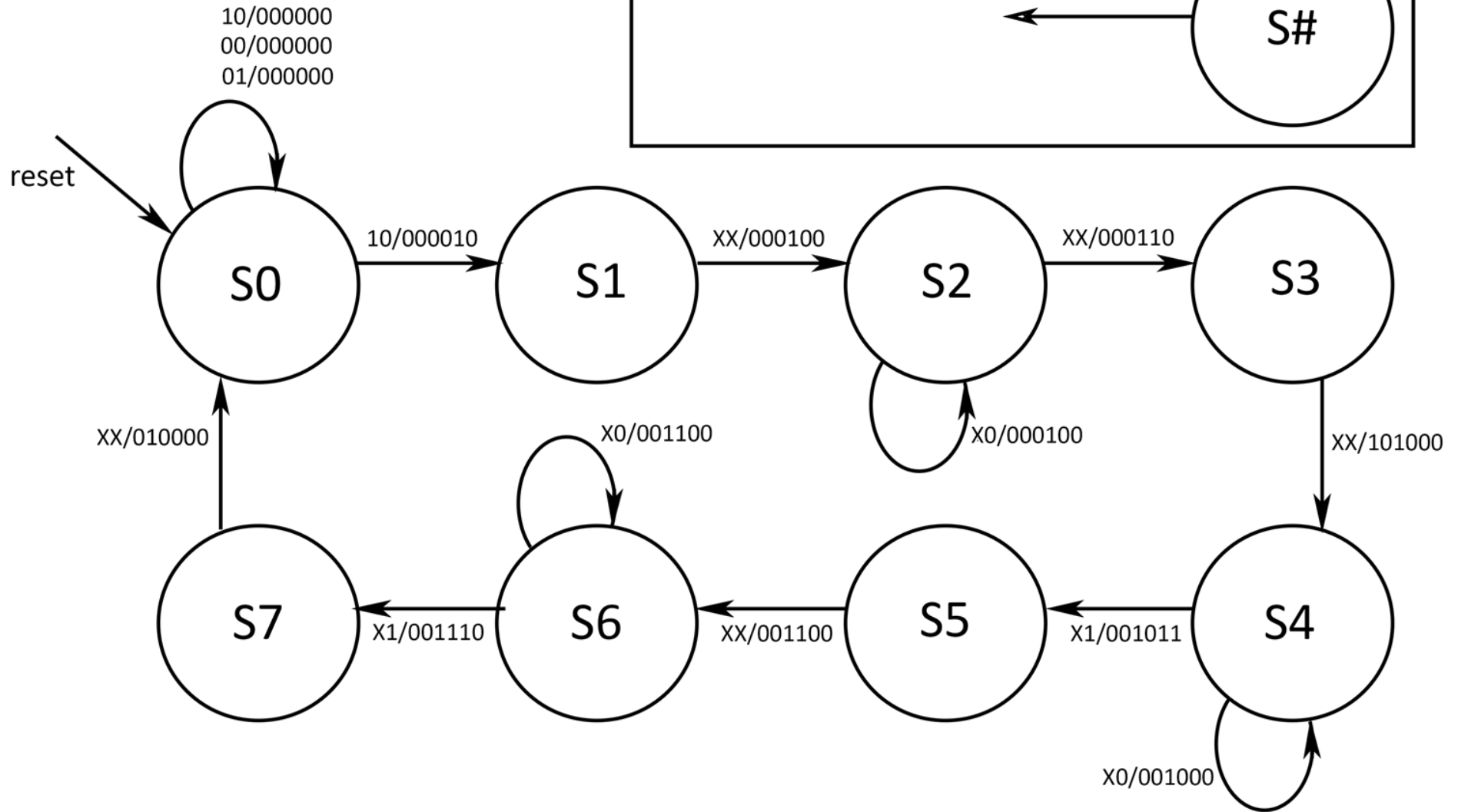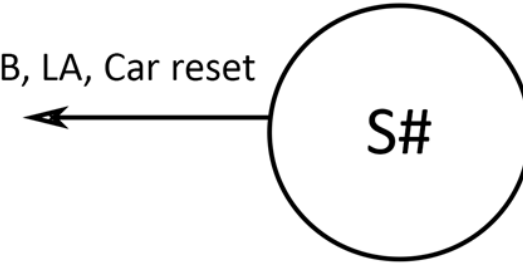
## Key:

waiting, done/T4, T8, LC, LB, LA, Car reset



# 4\_8 Timer Transition Table

CS	Q1	Q0	T4	T8	Q1+	Q0+	done
S0	0	0	0	0	0	0	1
S0	0	0	0	1	0	1	0
S0	0	0	1	0	1	1	0
S0	0	0	1	1	0	0	0
S1	0	1	0	0	1	0	0
S1	0	1	0	1	1	0	0
S1	0	1	1	0	1	0	0
S1	0	1	1	1	1	0	0
S2	1	0	0	0	1	1	0
S2	1	0	0	1	1	1	0
S2	1	0	1	0	1	1	0
S2	1	0	1	1	1	1	0
S3	1	1	0	0	0	0	0
S3	1	1	0	1	0	0	0
S3	1	1	1	0	0	0	0
S3	1	1	1	1	0	0	0

# 4\_8 Timer Minimized Transition Table

---

<b>CS</b>	<b>Q1</b>	<b>Q0</b>	<b>T4</b>	<b>T8</b>	<b>Q1+</b>	<b>Q0+</b>	<b>done</b>
S0	0	0	0	0	0	0	1
S0	0	0	0	1	0	1	0
S0	0	0	1	0	1	1	0
S0	0	0	1	1	0	0	0
S1	0	1	X	X	1	0	0
S2	1	0	X	X	1	1	0
S3	1	1	X	X	0	0	0

# Traffic Light Decoder Karnaugh Maps

		MR			
		LC	LB		
		00	01	11	10
LA	0	0	1	1	1
	1	0	1	1	1

$$MR = LC + LB$$

		MA			
		LC	LB		
		00	01	11	10
LA	0	0	0	0	0
	1	1	0	1	0

$$MA = LC.LB.LA + \neg LC.\neg LB.LA$$

		SR			
		LC	LB		
		00	01	11	10
LA	0	1	1	1	0
	1	1	1	1	0

$$SR = \neg LC + LB$$

		SA			
		LC	LB		
		00	01	11	10
LA	0	0	0	0	0
	1	0	1	0	1

$$SA = \neg LC.LB.LA + LC.\neg LB.LA$$

$$MG = \neg LC.\neg LB.\neg LA$$

$$SG = LC.\neg LB.\neg LA$$